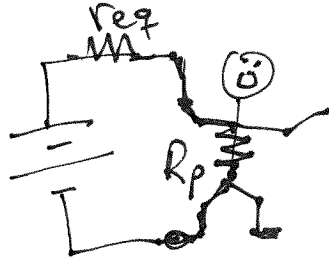


Ch10 Prob. 24

$$R_p = 10.0 \text{ k}\Omega$$

$$V = 20.0 \text{ kV}$$

a)



b)

$$r_{eq} = 2000 \Omega$$

Find the current through the body.

$$V = I \cdot R_p + I r_{eq} = I (R_p + r_{eq})$$

$$I = \frac{V}{R_p + r_{eq}} = \frac{20,000 \text{ V}}{10,000 \Omega + 2000 \Omega} = \frac{20,000 \text{ V}}{12,000 \Omega}$$

$$I = 1.67 \text{ A}$$

c) Find the power dissipated in the body

$$P = I_p \cdot V_p = I_p \cdot (I_p \cdot R_p) = I_p^2 R_p$$

$$= (1.67 \text{ A})^2 (10,000 \Omega) = 2.79 \times 10^4 \text{ W}$$

$$27.9 \text{ kW}$$

d)  $I_{max} = 1.00 \text{ mA}$

$$V = I_{max} (R_p + r_{new}) \rightarrow r_{new} = \frac{V}{I_{max}} - R_p$$

$$r_{new} = \frac{20,000 \text{ V}}{1.00 \times 10^{-3} \text{ A}} - 10,000 \Omega = 1.999 \times 10^7 \Omega$$

$$20 \text{ M}\Omega$$

e) This will not be effective at low resistance ~~device~~ devices since most of the power will be lost inside the power supply.