

Ch 10: Prob. 30

V = 48.0 V

R₁ = 24.0 Ω

R₂ = 96.0 Ω


a) Find current and power when the resistors are in series.

V - IR₁ - IR₂ = 0

V - I(R₁ + R₂) = 0

V = I(R₁ + R₂)

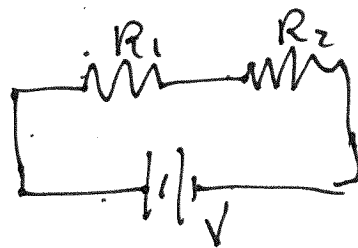I = V / (R₁ + R₂) = 48.0 V / (24 Ω + 96 Ω) = 0.40 A




P₁ = I₁² R₁ = (0.40 A)² (24.0 Ω) = 3.84 W

P₂ = I₂² R₂ = (0.40 A)² (96.0 Ω) = 15.36 W

b) Find current and power when the resistors are in parallel

1/R_p = 1/R₁ + 1/R₂ = 1/24 + 1/96

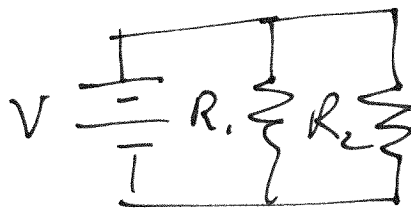

NOT necessary for this problem

~~1/R_p = 4/96 + 1/96 = 5/96~~

~~R_p = 96/5 = 19.2 Ω~~

1/R_p = 4/96 + 1/96 = 5/96 R_p = 96/5 = 19.2 Ω

I_{total} = V / R_p = 48 V / 19.2 Ω = 2.5 A

Notice the individual currents add up to this total current.

Now, 48 V is across each resistor, so

I₁ = V / R₁ = 48 V / 24 Ω = 2.0 A P₁ = I₁ · V = (2.0 A)(48 V) = 96 W

I₂ = V / R₂ = 48 V / 96 Ω = 0.5 A P₂ = I₂ · V = (0.5 A)(48 V) = 24 W