

Ch. 13 Prob 73

$$I_F = 0.50 \text{ A (full speed)} \quad V = 120 \text{ V}$$

$$I_s = 2.00 \text{ A (starting)}$$

$$R_A = 10 \Omega \text{ (armature coils)}$$

a) Find the resistance of the field coils.

Assume the armature + field coils are in series. When starting, there is no back emf so all of the external voltage drops across the coils.

$$\text{so } V = I_s (R_A + R_F) \rightarrow \frac{V}{I_s} - R_A = R_F$$

$$R_F = \frac{120 \text{ V}}{2.0 \text{ A}} - 10 \Omega = \boxed{50 \Omega}$$

b) Find the back emf when the motor is running.

The total voltage experienced by the coils is the difference between external voltage and the emf of the coils.

$$\text{so } V - \mathcal{E} = I_f (R_A + R_F)$$

$$V - I_f (R_A + R_F) = \mathcal{E}$$

$$\mathcal{E} = 120 - (0.50 \text{ A})(10 \Omega + 50 \Omega) = \boxed{90 \text{ V}}$$

c) Find the back emf when 1.0 A current is drawn.

$$\mathcal{E} = V - I (R_A + R_F)$$

$$= 120 \text{ V} - (1.0 \text{ A})(10 \Omega + 50 \Omega)$$

$$\boxed{\mathcal{E} = 60 \text{ V}}$$