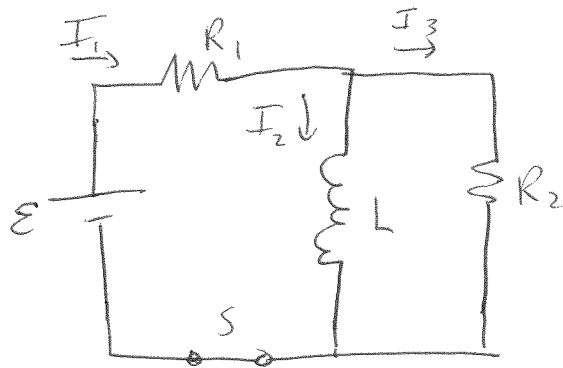


Ch 14, Prob 58

#1

Find $I_1, I_2 + I_3$ when



a) Switch is first closed

Initially no current is flowing ~~to~~ through the inductor and it will generate a ~~big~~ voltage to keep it that way

∴ $V_L = V_{R_2}$
and
 $I_2 = 0A$

By Kirchoff's Law
 $I_1 = I_2 + I_3 \rightarrow I_1 = I_3$
 $\epsilon - I_1 R_1 - I_3 R_3 = 0$

so $\epsilon - I_1 R_1 - I_1 R_3 = 0$

$$\epsilon = I_1 (R_1 + R_3) \Rightarrow \begin{cases} I_1 = \frac{\epsilon}{R_1 + R_3} \\ I_2 = 0 \\ I_3 = \frac{\epsilon}{R_1 + R_3} \end{cases}$$

b) Steady state value

If current is not changing, then the voltage across the inductor is 0.

so $V_L = 0$ and $V_{R_2} = 0$

But $V_{R_2} = I_3 R_2 \therefore I_3 = 0$

Since $I_1 = I_2 + I_3$ Then $I_1 = I_2$

By Kirchoff's law

$\epsilon - I_1 R_1 - V_L = 0$

$\epsilon - I_1 R_1 = 0 \rightarrow I_1 = \frac{\epsilon}{R_1}$

so $\begin{cases} I_1 = \frac{\epsilon}{R_1} \\ I_2 = \frac{\epsilon}{R_1} \\ I_3 = 0 \end{cases}$

c) Instant after the switch is reopened

Since before the switch is opened

$$V_L = 0$$

you would think everything is zero; however,

before the switch is opened $I_2 = \frac{\mathcal{E}}{R_1}$

After the switch is opened, the inductor maintains the current.

with the switch open $I_1 = 0$

$$I_1 = I_2 + I_3 = 0 \quad \therefore I_2 = -I_3$$

If $I_2 = \frac{\mathcal{E}}{R_1}$, then $I_3 = -\frac{\mathcal{E}}{R_1}$