

Ch. 15 Prob. 20

$$f = 1000 \text{ Hz}$$

$$L = 5.0 \text{ mH}$$

$$\omega = 2\pi \cdot f$$

$$= 2\pi (1000 \text{ Hz})$$

$$= 6283 \frac{\text{rad}}{\text{s}}$$

$$X_C = X_L$$

Find The capacitor value.

$$\text{since } X_C = \frac{1}{\omega C} \quad + \quad X_L = \omega L$$

Then

$$\frac{1}{\omega C} = \omega L$$

with algebra

$$C = \frac{1}{\omega^2 L} = \frac{1}{\left(6283 \frac{\text{rad}}{\text{s}}\right)^2 (5.0 \times 10^{-3} \text{ H})}$$

$$= 5.07 \times 10^{-6} \text{ F}$$

$$C = 5.07 \mu\text{F}$$