

Ch. 15 Prob. 22

$$C = 25 \mu\text{F}$$

$$v = (160 \text{ V}) \sin(120\pi t)$$

a) Find The reactance.

for a capacitor $X_c = \frac{1}{\omega C} = \frac{1}{(120\pi)(25 \times 10^{-6} \text{ F})}$

$$X_c = 106 \Omega$$

b) write an expression for the current.
In a capacitor $i = \frac{v}{X_c} \sin(\omega t - \phi)$ where $\phi = -\frac{\pi}{2}$

$$i = \frac{v}{X_c} = \frac{(160 \text{ V}) \sin(120\pi t + \frac{\pi}{2})}{106 \Omega}$$

$$i = (1.51 \text{ A}) \sin(120\pi t + \frac{\pi}{2})$$

amplitude

ϕ - negative phase shift

Current peaks before voltage