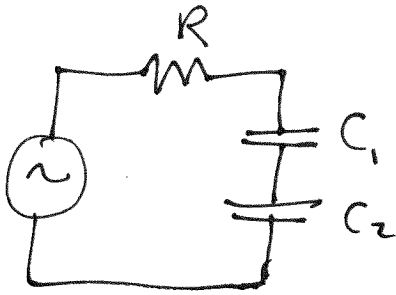


Ch. 15 Prob. 24



$$R = 50 \Omega$$

$$C_1 = 5.0 \mu\text{F} = 5.0 \times 10^{-6} \text{F}$$

$$C_2 = 10 \mu\text{F} = 10 \times 10^{-6} \text{F}$$

$$f = 2.0 \text{ kHz}$$

$C_1 + C_2$ are in series, so

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{5} + \frac{1}{10} = \frac{2}{10} + \frac{1}{10} = \frac{3}{10}$$

$$\therefore C_T = \frac{10}{3} = 3.33 \mu\text{F} = 3.33 \times 10^{-6} \text{F}$$

$$\begin{aligned} \omega &= 2\pi f = 2\pi (2,000 \text{ Hz}) = 4000\pi \frac{\text{rad}}{\text{s}} \\ &= 12,570 \frac{\text{rad}}{\text{s}} \end{aligned}$$

$$X_C = \frac{1}{\omega C_T} = \frac{1}{\left(12,570 \frac{\text{rad}}{\text{s}}\right) \left(3.33 \times 10^{-6} \text{F}\right)}$$

$$= 23.9 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(50)^2 + (0 - 23.9)^2}$$

$$Z = 55.4 \Omega$$