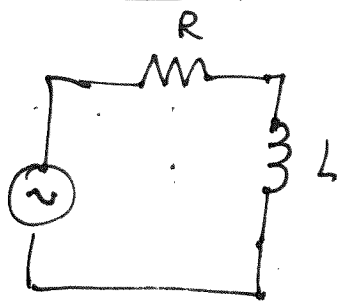


Ch. 15 Prob. 26



$$v(t) = V_0 \cos \omega t$$

$$V_0 = 120 \text{ V}$$

$$\omega = 120\pi \text{ rad/s}$$

$$R = 400 \Omega$$

$$L = 1.5 \text{ H}$$

a) What is the impedance of the circuit?

$$X_L = \omega L = (120\pi \frac{\text{rad}}{\text{s}})(1.5 \text{ H}) = \boxed{565 \Omega}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(400)^2 + (565 - 0)^2}$$

$$\boxed{Z = 692 \Omega}$$

b) What is the amplitude of the current

$$I_0 = \frac{V_0}{Z} = \frac{120 \text{ V}}{692 \Omega} = \boxed{0.173 \text{ A}}$$

c) Write an expression for the current through the resistor

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\left(\frac{565 - 0}{400}\right) = +0.955 \text{ rad}$$

$$\boxed{i(t) = (0.173 \text{ A}) \cos(120\pi t - 0.955)}$$

d) Write voltage across the resistor and the inductor

$$V_R = i \cdot R = (0.173 \text{ A}) \cos(120\pi t - 0.955)(400 \Omega)$$

$$\boxed{V_R = (69.2 \text{ V}) \cos(120\pi t - 0.955)}$$

Voltage leads current by  $\pi/2$  in the inductor so  $\phi = \frac{\pi}{2} - 0.955$

$$V_L = i \cdot X_L = (0.173 \text{ A}) \cos(120\pi t - 0.955)(565)$$

$$\boxed{V_L = (97.7 \text{ V}) \cos(120\pi t + 0.616)}$$

$$= 0.616 \text{ rad}$$