

Ch. 15 Prob 33

$$V_0 = 100 \text{ V}$$

$$V_{rms} = \frac{100 \text{ V}}{\sqrt{2}} = 70.7 \text{ V} \quad \textcircled{\#1}$$

$$f = 500 \text{ Hz}$$

$$\omega = 2\pi f = 2\pi(500) = 1000\pi \text{ rad/s}$$

$$R = 500 \Omega$$

$$L = 0.20 \text{ H}$$

Find The power dissipated in The resistor.

a) For $C = 2.0 \mu\text{F}$

$$X_L = \omega L = (1000\pi)(0.20) = 628 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(2 \times 10^{-6})(1000\pi)} = 159 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(500)^2 + (628 - 159)^2} = 686 \Omega$$

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{70.7 \text{ V}}{686 \Omega} = 0.103 \text{ A}$$

$$V_R = I_{rms} \cdot R = (0.103 \text{ A})(500 \Omega) = 51.5 \text{ V}$$

No phase shift in resistor

$$P_R = I_{rms} \cdot V_{rms} = (0.103 \text{ A})(51.5 \text{ V})$$

$$P_R = 5.31 \text{ W}$$

Textbook solution incorrect.

Look at The source

phase shift between V & I

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right) = \tan^{-1} \left(\frac{628 - 159}{500} \right) = 0.75 \text{ rad}$$

$$P_{source} = I_{rms} V_{rms} \cos \phi = (0.103 \text{ A})(70.7 \text{ V}) \cos(0.75 \text{ rad})$$

$$P_{source} = 5.32 \text{ W}$$

Notice The power by The source equals power used by The resistor.

b) For $C = 0.20 \mu\text{F}$

$$X_L = \omega L = (1000\pi)(0.20) = 628 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(1000\pi)(2 \times 10^{-7})} = 1592 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(500)^2 + (628 - 1592)^2} = 1086 \Omega$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{70.7 \text{ V}}{1086 \Omega} = 0.0651 \text{ A}$$

$$V_R = I_{\text{rms}} \cdot R = (0.0651 \text{ A})(500 \Omega) = 32.6 \text{ V}$$

$$P_R = I_{\text{rms}} \cdot V_{\text{rms}} = (0.0651 \text{ A})(32.6 \text{ V})$$

$$P_R = 2.12 \text{ W}$$

← Textbook
answer
incorrect