

Ch. 15 Prob. 55

$$I_L = 4.24 \text{ A}$$

Find The value of The resistor

The current given is an amplitude, or peak value.

The amplitude of the voltage is  $V_0 = 50 \text{ V}$

Since the inductor is in series with the inductor  
The power supply current is the same as the inductor


$$\therefore V_0 = I_0 \cdot Z \rightarrow Z = \frac{V_0}{I_0} = \frac{50 \text{ V}}{4.24 \text{ A}} = 11.8 \Omega$$

The angular frequency is

$$\omega = 120\pi \frac{\text{rad}}{\text{s}}$$

The equivalent single capacitor  
is due to the 2 capacitors in  
parallel. Therefore

$$C = 200 + 400 = 600 \mu\text{F}$$

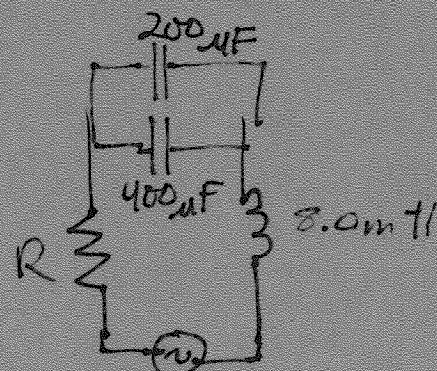

Capacitive reactance is

$$X_C = \frac{1}{\omega C} = \frac{1}{(120\pi)(600 \times 10^{-6})}$$

Inductive reactance is

$$X_L = \omega L = (120\pi)(8.0 \times 10^{-3})$$

Since  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$Z^2 = R^2 + (X_L - X_C)^2$$

$$R^2 = Z^2 - (X_L - X_C)^2 \rightarrow R = \sqrt{Z^2 - (X_L - X_C)^2}$$

$$R = \sqrt{(11.8)^2 - (3.02 - 4.42)^2} = 11.7 \Omega$$