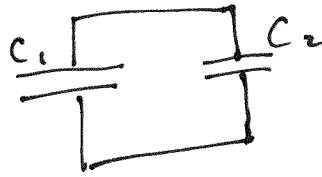


Ch. 8 Prob. 38

$$C_1 = 40 \text{ pF}$$

$$V_0 = 500 \text{ V}$$

$$C_2 = 10 \text{ pF}$$



a) Initially the first capacitor has the following charge

$$C_1 = \frac{Q_0}{V_0} \rightarrow Q_0 = C_1 V_0 = (40 \text{ pF})(500 \text{ V}) = \underline{\underline{20,000 \text{ pC}}}$$

b) When this capacitor is attached to the second capacitor, some of the charge will be transferred ~~to~~ from the first capacitor to the second one. The transfer will continue until the voltage across each capacitor matches.

$$C_1 = \frac{Q_1}{V_1} \rightarrow V_1 = \frac{Q_1}{C_1} \quad \text{where } V_1 \text{ is the new voltage across the first capacitor and } Q_1 \text{ is the new amount of charge on the first capacitor.}$$

Likewise for the second capacitor

$$V_2 = \frac{Q_2}{C_2}$$

Set these equations equal to each other

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \rightarrow Q_1 = \frac{C_1}{C_2} Q_2$$

Now the original charge must equal the sum of the new charge on each capacitor

$$\text{so } Q_0 = Q_1 + Q_2 \rightarrow Q_0 = \frac{C_1}{C_2} Q_2 + Q_2$$

$$\text{Now } C_1 V_0 = C_1 V_1 + C_2 V_2 \neq Q_0 = \left(1 + \frac{C_1}{C_2}\right) Q_2$$

$$Q_2 = \frac{Q_0}{\left(1 + \frac{C_1}{C_2}\right)} = \frac{20,000 \text{ pC}}{1 + \frac{40 \text{ pF}}{10 \text{ pF}}} = \frac{20,000 \text{ pC}}{5}$$

$$\boxed{Q_2 = 4,000 \text{ pC}}$$

charge on the first capacitor is then

$$Q_1 = \frac{C_1}{C_2} Q_2 = \left(\frac{40 \text{ pF}}{10 \text{ pF}}\right) 4,000 \text{ pC} \\ = 4 (4,000 \text{ pC}) = \boxed{16,000 \text{ pC}}$$

c) The new voltage is then

$$V_2 = \frac{Q_2}{C_2} = \frac{4,000 \text{ pC}}{10 \text{ pF}} = 200 \text{ V}$$

$$V_1 = \frac{Q_1}{C_1} = \frac{16,000 \text{ pC}}{40 \text{ pF}} = \boxed{400 \text{ V}}$$

Notice: both voltages ~~match~~ match.