



Ch. 8 Prob 46

$$V = 9.00V$$

$$C_1 = 2.00 \mu F$$

$$C_2 = 7.40 \mu F$$

a) Place the capacitors in series

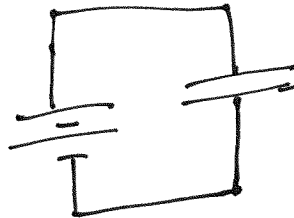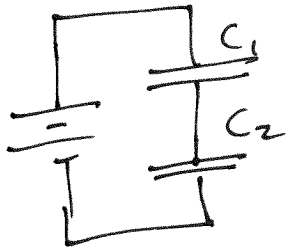

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C_s} = \frac{1}{2.00 \mu F} + \frac{1}{7.40 \mu F}$$

$$\frac{1}{C_s} = 0.635 \frac{1}{\mu F}$$

$$C_s = 1.57 \mu F$$

Charge will be the same in each capacitor because they are connected in series


$$C = \frac{Q}{V} \rightarrow Q = C \cdot V$$

$$Q = (1.57 \times 10^{-6} F)(9.00V) = 1.41 \times 10^{-5} C = \boxed{14.1 \mu C}$$

Energy on the collection of capacitors is

$$U_c = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(1.41 \times 10^{-5} C)^2}{(1.57 \times 10^{-6} F)} = 6.33 \times 10^{-5} J = \boxed{63.3 \mu J}$$

b) Place the capacitors in parallel

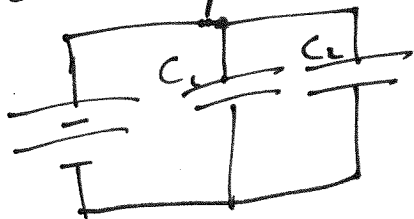

$$C_p = C_1 + C_2$$

$$= 2.00 \mu F + 7.40 \mu F$$

$$= 9.40 \mu F$$

Voltage is the same across both capacitors, the charge

total charge on each capacitor is

$$Q = C \cdot V = (9.40 \times 10^{-6} F)(9.00V)$$

$$Q = 8.46 \times 10^{-5} C = \boxed{84.6 \mu C}$$

Energy stored is

$$U_c = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(8.46 \times 10^{-5} C)^2}{(9.40 \times 10^{-6} F)} = 3.81 \times 10^{-4} J = \boxed{381 \mu J}$$